

DESIGN AND IMPLEMENTATION OF HACK CPU AND SYNCHRONOUS COUNTER THAT COUNTS DOWN FROM DECIMAL DIGIT 9 TO 0

A PROJECT REPORT

Submitted by

CHAITANYA VARMA	-	CB.SC.U4AIE24017
HARSHITH REDDY	-	CB.SC.U4AIE24018
JISHNU TEJA DANDAMUDI	-	CB.SC.U4AIE24019
JIVITES DAMODAR	-	CB.SC.U4AIE24020



**CENTER FOR COMPUTATIONAL ENGINEERING AND
NETWORKING
AMRITA SCHOOL OF ARTIFICIAL INTELLIGENCE
COIMBATORE-641112
2024**

**AMRITA SCHOOL OF ARTIFICIAL INTELLIGENCE
AMRITA VISHWA VIDYAPEETHAM
COIMBATORE-641112**

DECLARATION

We, **Chaitanya Varma – CB.SC.U4AIE24017, Harshith Reddy - CB.SC.U4AIE24018, Jishnu Teja Dandamudi - CB.SC.U4AIE24019 and Jivites Damodar - CB.SC.U4AIE24020**, hereby declare that the project work entitled “**DESIGNING AND IMPLEMENTATION OF HACK CPU AND SYNCHRONOUS COUNTER THAT COUNTS DOWN FROM DECIMAL DIGIT 9 TO 0**” is the record of the original work done by us under the guidance of **Dr. Lekshmi C. R.**, Assistant Professor, Department of Artificial Intelligence, Amrita Vishwa Vidyapeetham, Coimbatore.

Chaitanya Varma - CB.SC.U4AIE24017

Harshith Reddy - CB.SC.U4AIE24018

Jishnu Teja Dandamudi - CB.SC.U4AIE24019 Jivites Damodar - CB.SC.U4AIE24020

Place: Coimbatore – 641112

Date:

COUNTERSIGNED

Dr. Lekshmi C R,
Assistant Professor,
Department of Artificial Intelligence

TABLE OF CONTENTS

<u>S. No</u>	<u>TOPIC</u>	<u>Pg. No</u>
1. Introduction		
a.	Hardware Description Language	4
b.	Hardware Simulation	4
c.	HACK CPU	21
d.	MOD 10	30
2. List of Gates Used		5
3. Chips with their hdl codes with their truth tables		
•	And	7
•	Or	8
•	Not	9
•	And16	10
•	Or16	11
•	Not16	12
•	Or8Way	13
•	Mux	14
•	Mux16	15
•	Xor	16
•	Or16Way	17
•	Half Adder	18
•	Full Adder	19
•	Add16	20
•	Inc16	21
•	ALU	24
•	Bit	26
•	Register	26
•	PC	27
•	Ram8	27
•	Ram64	27
•	HACK CPU	28
•	And3	34
•	JK Flip Flop using D Flip Flop	34
•	MOD10 Synchronous Down Counter	35

4. List of Figures

• And	7
• Or	8
• Not	9
• And16	10
• Or16	11
• Not16	12
• Or8Way	13
• Mux	14
• Mux16	15
• Xor	16
• Or16Way	17
• Half Adder	18
• Full Adder	19
• Add16	20
• Inc16	21
• Top Most Computer HACK CHIP	23
• Design of HACK CPU	23
• ALU	24
• HACK CPU	27
• Block diagram for mod-10 synchronous down counter	32
• State Diagram for MOD10	33
• K-MAPS for JK Flip Flops Used	33

5. Outputs

• ALU	25
• HACK CPU	29
• MOD10	36

6. Conclusion

37

INTRODUCTION

1. HARDWARE DESCRIPTION LANGUAGE(HDL):

Today, hardware designers no longer build anything with their bare hands. Instead, they plan and optimize the chip architecture on a computer workstation, using structured modelling formalisms like Hardware Description Language, or HDL (also known as VHDL, where V stands for Virtual). The designer specifies the chip structure by writing an HDL program, which is then subjected to a rigorous battery of tests. These tests are carried out virtually, using computer simulation: A special software tool, called a hardware simulator, takes the HDL program as input and builds an image of the modelled chip in memory. Next, the designer can instruct the simulator to test the virtual chip on various sets of inputs, generating simulated chip outputs. The outputs can then be compared to the desired results, as mandated by the client who ordered the chip built. In addition to testing the chip's correctness, the hardware designer will typically be interested in a variety of parameters such as speed of computation, energy consumption, and the overall cost implied by the chip design. All these parameters can be simulated and quantified by the hardware simulator, helping the designer optimize the design until the simulated chip delivers desired cost/performance levels. Thus, using HDL, one can completely plan, debug, and optimize the entire chip before a single penny is spent on actual production. When the HDL program is deemed complete, that is, when the performance of the simulated chip satisfies the client who ordered it, the HDL program can become the blueprint from which many copies of the physical chip can be stamped in silicon. This final step in the chip life cycle - from an optimized HDL program to mass production - is typically out-sourced to companies that specialize in chip fabrication, using one switching technology or another.

2. HARDWARE SIMULATION:

Since HDL is a hardware construction language, the process of writing and debugging HDL programs is quite similar to software development. The main difference is that instead of writing code in a language like Java, we write it in HDL, and instead of using a compiler to translate and test the code, we use a hardware simulator. The hardware simulator is a computer program that knows how to parse and interpret HDL code, turn it into an executable representation, and test it according to the specifications of a given test script. There exist many commercial hardware simulators on the market, and these vary greatly in terms of cost, complexity, and ease of use. Together with this book we provide a simple (and free!) hardware simulator that is sufficiently powerful to support sophisticated hardware design projects. In particular, the simulator provides all the necessary tools for building, testing, and integrating all the chips presented in the book, leading to the construction of a general-purpose computer.

LIST OF GATES USED IN THE OVERALL PROJECT

1. And
2. Or
3. Not
4. And16
5. Or16
6. Not16
7. Or8Way
8. Mux
9. Mux16
10. Xor
11. Or16Way
12. Half Adder
13. Full Adder
14. Add16
15. Inc16

CHIPS USED

1. AND

The And function returns 1 (true) only when both of the inputs are 1 (true).

2 - input AND gate



```
CHIP And {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Nand(a=a, b=b, out=temp);  
    Not(in=temp, out=out);  
}
```

	a		b		out	
	0		0		0	
	0		1		0	
	1		0		0	
	1		1		1	

2. OR

The Or function returns 1 (true) when either of the inputs are 1 (true).

2 - input OR gate




```
CHIP Or {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not(in=a, out=nota);  
    Not(in=b, out=notb);  
    Nand(a=nota, b=notb, out=out);  
}
```

a	b	out
0	0	0
0	1	1
1	0	1
1	1	1

 3. NOT

The single-input Not Gate, also referred as Inverter, inverts the value of input.



```
CHIP Not {  
    IN in;  
    OUT out;  
  
    PARTS:  
    Nand(a=in, b=in, out=out);  
}
```

in	out
0	1
1	0

4. AND16

An 16-bit And Chip applies the Boolean operation And to every one of the bits in its 16-bit input bus.

```
CHIP And16 {
  IN a[16], b[16];
  OUT out[16];

  PARTS:
    And(a=a[0], b=b[0], out=out[0]);
    And(a=a[1], b=b[1], out=out[1]);
    And(a=a[2], b=b[2], out=out[2]);
    And(a=a[3], b=b[3], out=out[3]);
    And(a=a[4], b=b[4], out=out[4]);
    And(a=a[5], b=b[5], out=out[5]);
    And(a=a[6], b=b[6], out=out[6]);
    And(a=a[7], b=b[7], out=out[7]);
    And(a=a[8], b=b[8], out=out[8]);
    And(a=a[9], b=b[9], out=out[9]);
    And(a=a[10], b=b[10], out=out[10]);
    And(a=a[11], b=b[11], out=out[11]);
    And(a=a[12], b=b[12], out=out[12]);
    And(a=a[13], b=b[13], out=out[13]);
    And(a=a[14], b=b[14], out=out[14]);
    And(a=a[15], b=b[15], out=out[15]);
}
```

a	b	out
0000000000000000	0000000000000000	0000000000000000
0000000000000000	1111111111111111	0000000000000000
1111111111111111	1111111111111111	1111111111111111
1010101010101010	0101010101010101	0000000000000000
0011110011000011	0000111111110000	0000110011000000
0001001000110100	1001100001110110	0001000000110100

5. OR16

An 16-bit Or Chip applies the Boolean operation Or to every one of the bits in its 16-bit input bus.

```
CHIP Or16 {  
    IN a[16], b[16];  
    OUT out[16];  
  
    PARTS:  
    Or(a=a[0], b=b[0], out=out[0]);  
    Or(a=a[1], b=b[1], out=out[1]);  
    Or(a=a[2], b=b[2], out=out[2]);  
    Or(a=a[3], b=b[3], out=out[3]);  
    Or(a=a[4], b=b[4], out=out[4]);  
    Or(a=a[5], b=b[5], out=out[5]);  
    Or(a=a[6], b=b[6], out=out[6]);  
    Or(a=a[7], b=b[7], out=out[7]);  
    Or(a=a[8], b=b[8], out=out[8]);  
    Or(a=a[9], b=b[9], out=out[9]);  
    Or(a=a[10], b=b[10], out=out[10]);  
    Or(a=a[11], b=b[11], out=out[11]);  
    Or(a=a[12], b=b[12], out=out[12]);  
    Or(a=a[13], b=b[13], out=out[13]);  
    Or(a=a[14], b=b[14], out=out[14]);  
    Or(a=a[15], b=b[15], out=out[15]);  
}
```

a	b	out
0000000000000000	0000000000000000	0000000000000000
0000000000000000	1111111111111111	1111111111111111
1111111111111111	1111111111111111	1111111111111111
1010101010101010	0101010101010101	1111111111111111
0011110011000011	0000111111110000	0011111111110011
0001001000110100	1001100001110110	1001101001110110

6. NOT16

Unlike Not gate, Not16 takes 16-bit input, inverts each bit and produces output. In other words, An 16-bit Not Chip applies the Boolean operation Not to every one of the bits in its 16-bit input bus.

```
CHIP Not16 {
    IN in[16];
    OUT out[16];

    PARTS:
        Not(in=in[0], out=out[0]);
        Not(in=in[1], out=out[1]);
        Not(in=in[2], out=out[2]);
        Not(in=in[3], out=out[3]);
        Not(in=in[4], out=out[4]);
        Not(in=in[5], out=out[5]);
        Not(in=in[6], out=out[6]);
        Not(in=in[7], out=out[7]);
        Not(in=in[8], out=out[8]);
        Not(in=in[9], out=out[9]);
        Not(in=in[10], out=out[10]);
        Not(in=in[11], out=out[11]);
        Not(in=in[12], out=out[12]);
        Not(in=in[13], out=out[13]);
        Not(in=in[14], out=out[14]);
        Not(in=in[15], out=out[15]);
}
```

in	out
0000000000000000	1111111111111111
1111111111111111	0000000000000000
1010101010101010	0101010101010101
0011110011000011	1100001100111100
0001001000110100	1110110111001011

7. OR8WAY

An 8-way or gate outputs 1 when at least one bit of its 16-bit input is 1. Unlike n-bit input logic gates, n-way logic gates use the same output iteratively over the Boolean operation, which means, it uses the previous output as input for the next similar Boolean operation.

```
CHIP Or8Way {
  IN in[8];
  OUT out;


  PARTS:
    Or(a=in[0], b=in[1], out=t1);
    Or(a=t1, b=in[2], out=t2);
    Or(a=t2, b=in[3], out=t3);
    Or(a=t3, b=in[4], out=t4);
    Or(a=t4, b=in[5], out=t5);
    Or(a=t5, b=in[6], out=t6);
    Or(a=t6, b=in[7], out=out);
}
```

	in		out	
	00000000		0	
	11111111		1	
	00010000		1	
	00000001		1	
	00100110		1	

 8. MUX

A Multiplexor, also known as Selector, is a three-input bit gate that uses one of the inputs called "selection bit" to select one of the given two inputs for outputting them.

The name multiplexor was adopted from communications systems, where similar devices are used to serialize (multiplex) several input signals over a single output wire.



```
CHIP Mux {
  IN a, b, sel;
  OUT out;

  PARTS:
    Not(in=sel, out=notsel);
    And(a=a, b=notsel, out=t1);
    And(a=b, b=sel, out=t2);
    Or(a=t1, b=t2, out=out);
}
```

a	b	sel	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

9. MUX16

An 16-bit multiplexor is almost similar to the Multiplexor Chip described previously, except that both inputs are each 16-bit wide, while the selector is a single bit.

```
CHIP Mux16 {
  IN a[16], b[16], sel;
  OUT out[16];

  PARTS:
    Mux(a=a[0], b=b[0], sel=sel, out=out[0]);
    Mux(a=a[1], b=b[1], sel=sel, out=out[1]);
    Mux(a=a[2], b=b[2], sel=sel, out=out[2]);
    Mux(a=a[3], b=b[3], sel=sel, out=out[3]);
    Mux(a=a[4], b=b[4], sel=sel, out=out[4]);
    Mux(a=a[5], b=b[5], sel=sel, out=out[5]);
    Mux(a=a[6], b=b[6], sel=sel, out=out[6]);
    Mux(a=a[7], b=b[7], sel=sel, out=out[7]);
    Mux(a=a[8], b=b[8], sel=sel, out=out[8]);
    Mux(a=a[9], b=b[9], sel=sel, out=out[9]);
    Mux(a=a[10], b=b[10], sel=sel, out=out[10]);
    Mux(a=a[11], b=b[11], sel=sel, out=out[11]);
    Mux(a=a[12], b=b[12], sel=sel, out=out[12]);
    Mux(a=a[13], b=b[13], sel=sel, out=out[13]);
    Mux(a=a[14], b=b[14], sel=sel, out=out[14]);
    Mux(a=a[15], b=b[15], sel=sel, out=out[15]);
}
```

a	b	sel	out
0000000000000000	0000000000000000	0	0000000000000000
0000000000000000	0000000000000000	1	0000000000000000
0000000000000000	0001001000110100	0	0000000000000000
0000000000000000	0001001000110100	1	0001001000110100
1001100001110110	0000000000000000	0	1001100001110110
1001100001110110	0000000000000000	1	0000000000000000
1010101010101010	0101010101010101	0	1010101010101010
1010101010101010	0101010101010101	1	0101010101010101

10. XOR

The Xor function, also known as Exclusive-OR, returns 1 (true) when either of the inputs are same (both are 0 or both are 1 simultaneously).

Exclusive-OR gate



```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not(in=a, out=nota);  
    Not(in=b, out=notb);  
  
    And(a=a, b=notb, out=w1);  
    And(a=nota, b=b, out=w2);  
  
    Or(a=w1, b=w2, out=out);  
}
```

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

11. OR16WAY

```
CHIP Or16Way {
    IN
        in[16];
    OUT
        out;

    PARTS:
        Or8Way(in=in[0..7], out=t1);
        Or8Way(in=in[8..15], out=t2);
        Or(a=t1, b=t2, out=out);
}
```

[illegible]

12. HALF ADDER

The chip used to add two n-bit numbers is known as Adder, also known as n-bit Adder.

Half Adder chip is used to add 2-bits.




```
CHIP HalfAdder {  
    IN a, b;      // 1-bit inputs  
    OUT sum,      // Right bit of a + b  
        carry;   // Left bit of a + b  
  
    PARTS:  
    Xor(a=a, b=b, out=sum);  
    And(a=a, b=b, out=carry);  
}
```

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

13. FULL ADDER

Full Adder chip is used to add 3-bits.

 


```
CHIP FullAdder {  
    IN a, b, c; // 1-bit inputs  
    OUT sum,    // Right bit of a + b + c  
        carry; // Left bit of a + b + c  
  
    PARTS:  
    HalfAdder(a=a, b=b, sum=w1, carry=c1);  
    HalfAdder(a=w1, b=c, sum=sum, carry=c2);  
    Or(a=c1, b=c2, out=carry);  
}
```

a	b	c	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

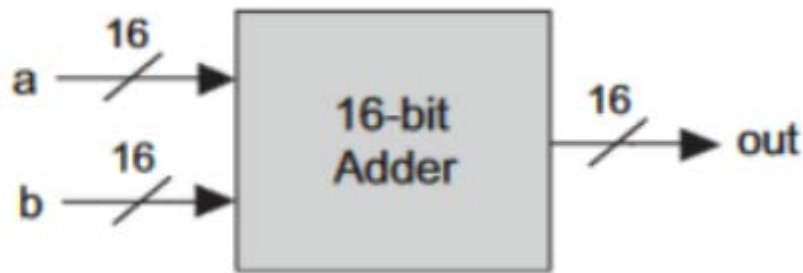14. ADD16

16-bit Adder chip is used to add two 16-bit numbers.




```
CHIP Add16 {
  IN a[16], b[16];
  OUT out[16];

  PARTS:
    HalfAdder(a=a[0], b=b[0], sum=out[0], carry=c1);
    FullAdder(a=a[1], b=b[1], c=c1, sum=out[1], carry=c2);
    FullAdder(a=a[2], b=b[2], c=c2, sum=out[2], carry=c3);
    FullAdder(a=a[3], b=b[3], c=c3, sum=out[3], carry=c4);
    FullAdder(a=a[4], b=b[4], c=c4, sum=out[4], carry=c5);
    FullAdder(a=a[5], b=b[5], c=c5, sum=out[5], carry=c6);
    FullAdder(a=a[6], b=b[6], c=c6, sum=out[6], carry=c7);
    FullAdder(a=a[7], b=b[7], c=c7, sum=out[7], carry=c8);
    FullAdder(a=a[8], b=b[8], c=c8, sum=out[8], carry=c9);
    FullAdder(a=a[9], b=b[9], c=c9, sum=out[9], carry=c10);
    FullAdder(a=a[10], b=b[10], c=c10, sum=out[10], carry=c11);
    FullAdder(a=a[11], b=b[11], c=c11, sum=out[11], carry=c12);
    FullAdder(a=a[12], b=b[12], c=c12, sum=out[12], carry=c13);
    FullAdder(a=a[13], b=b[13], c=c13, sum=out[13], carry=c14);
    FullAdder(a=a[14], b=b[14], c=c14, sum=out[14], carry=c15);
    FullAdder(a=a[15], b=b[15], c=c15, sum=out[15]);
}
```

a	b	out
0000000000000000	0000000000000000	0000000000000000
0000000000000000	1111111111111111	1111111111111111
1111111111111111	1111111111111111	1111111111111110
1010101010101010	0101010101010101	1111111111111111
0011110011000011	0000111111110000	0100110010110011
0001001000110100	1001100001110110	1010101010101010

 15. INC16

16-bit Incrementor chip is a special kind of Adder, used to increment a 16-bit input by 1.



4- Bit Binary Incrementer

```
CHIP Inc16 {  
    IN in[16];  
    OUT out[16];  
  
    PARTS:  
    Add16(a=in, b[0]=true, b[1..15]=false, out=out);  
}
```

in	out
0000000000000000	0000000000000001
1111111111111111	0000000000000000
00000000000000101	00000000000000110
1111111111111011	1111111111111100

DESIGNING AND IMPLEMENTING A 16 BIT HACK CPU

1. HACK CPU:

The Hack CPU consists of the ALU specified in chapter 2 and three registers called data register (D), address register (A), and program counter (PC). D and A are general-purpose 16-bit registers that can be manipulated by arithmetic and logical instructions like $A=D-1$, $D=D|A$, and so on, following the Hack machine language specified in chapter 4. While the D-register is used solely to store data values, the contents of the A-register can be interpreted in three different ways, depending on the instruction's context: as a data value, as a RAM address, or as a ROM address. The Hack machine language is based on two 16-bit command types. The address instruction has the format 0vvvvvvvvvvvvvvv, each v being 0 or 1. This instruction causes the computer to load the 15-bit constant vvv...v into the A-register. The compute instruction has the format 111acccccddjjj. The a- and c-bits instruct the ALU which function to compute, the d-bits instruct where to store the ALU output, and the j-bits specify an optional jump condition, all according to the Hack machine language specification. The computer architecture is wired in such a way that the output of the program counter (PC) chip is connected to the address input of the ROM chip. This way, the ROM chip always emits the word ROM[PC], namely, the contents of the instruction memory location whose address is "pointed at" by the PC. This value is called the current instruction.


2. Contents of HACK CPU:

The HACK CPU has the following key features:


- 16-bit word size: The CPU processes data in 16-bit chunks.
 - Registers: It includes a program counter (PC), instruction register (IR), and a set of general-purpose registers (R0 to R7).
 - ALU: An Arithmetic Logic Unit to perform arithmetic and logical operations.
 - Memory: Support for RAM and ROM.
 - Input/Output: Basic I/O operations through the RAM.
- a. Registers
 - Program Counter (PC): Points to the address of the next instruction.
 - Instruction Register (IR): Holds the current instruction being executed.
 - General-purpose registers (R0 to R7): For temporary data storage.
 - b. ALU Operations

The ALU supports several operations, such as:

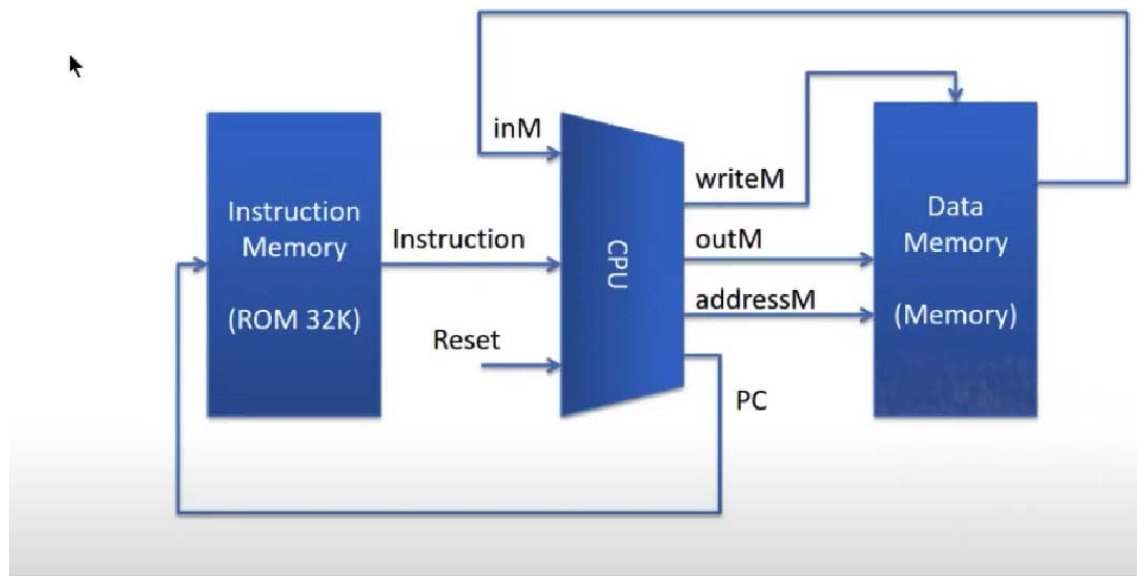 - Addition
 - Subtraction
 - Bitwise AND, OR, NOT
 - c. Control Unit
 - Decodes instructions and controls the execution of operations.
 - d. Memory
 - RAM: Stores data and instructions.
 - ROM: Stores the program to be executed.




CENTRAL PROCESSING UNIT

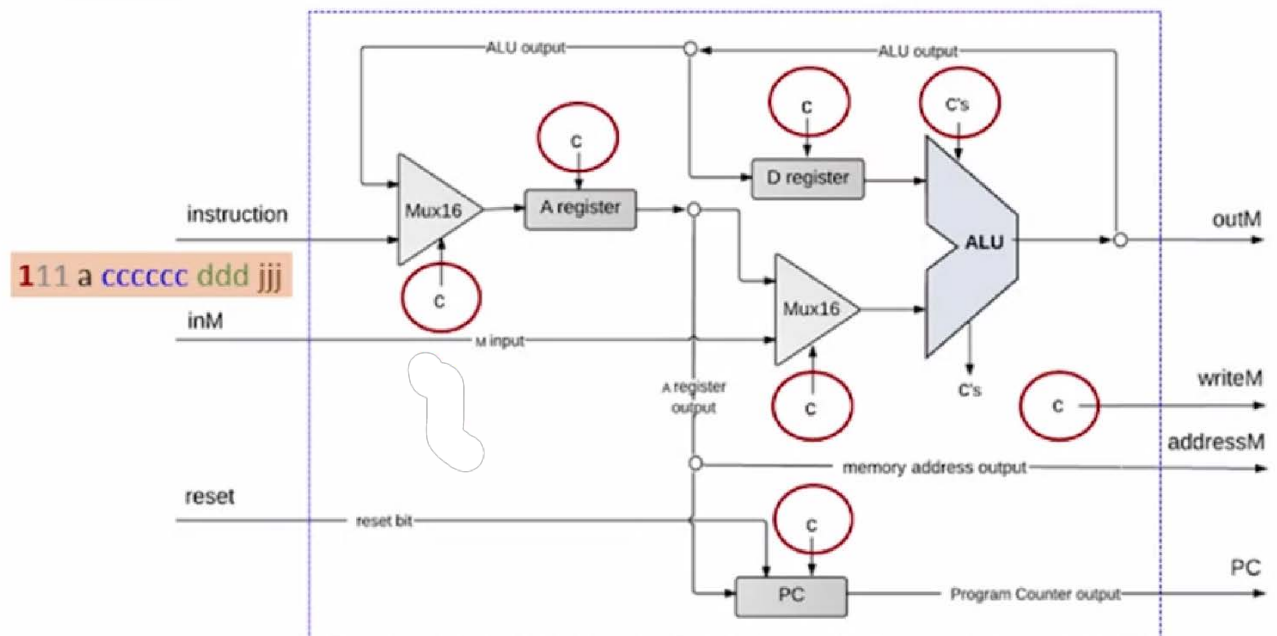

ALU

The Hack ALU computes a fixed set of functions on given two 16-bit inputs, out of which the function can be one of the possible eighteen functions.

 We instruct the ALU which function to compute using six input bits, called control bits to the selected binary values.



```
CHIP ALU {
    IN
        x[16], y[16], // 16-bit inputs
        zx, // zero the x input?
        nx, // negate the x input?
        zy, // zero the y input?
        ny, // negate the y input?
        f, // compute out = x + y (if f == 1) or out = x & y (if == 0)
        no; // negate the out output?

    OUT
        out[16], // 16-bit output
        zr, // 1 if (out == 0), 0 otherwise
        ng; // 1 if (out < 0), 0 otherwise

    PARTS:
        Mux16(a=x, b=false, sel=zx, out=x1);
        Not16(in=x1, out=notx1);
        Mux16(a=x1, b=notx1, sel=nx, out=tx);

        Mux16(a=y, b=false, sel=zy, out=y1);
        Not16(in=y1, out=noty1);
        Mux16(a=y1, b=noty1, sel=ny, out=ty);

        And16(a=tx, b=ty, out=tand);
        Add16(a=tx, b=ty, out=tadd);
        Mux16(a=tand, b=tadd, sel=f, out=t);

        Not16(in=t, out=nott);
        Mux16(a=t, b=nott, sel=no, out=out, out[15]=ng, out=o1);

        Or16Way(in=o1, out=notzr);
        Not(in=notzr, out=zr);
}
```


OUTPUT

x	y	zx	nx	zy	ny	f	no	out	zr	ng
0000000000000000	1111111111111111	1	0	1	0	1	0	0000000000000000	1	0
0000000000000000	1111111111111111	1	1	1	1	1	1	0000000000000001	0	0
0000000000000000	1111111111111111	1	1	1	0	1	0	1111111111111111	0	1
0000000000000000	1111111111111111	0	0	1	1	0	0	0000000000000000	1	0
0000000000000000	1111111111111111	1	1	0	0	0	0	1111111111111111	0	1
0000000000000000	1111111111111111	0	0	1	1	0	1	1111111111111111	0	1
0000000000000000	1111111111111111	1	1	0	0	0	1	0000000000000000	1	0
0000000000000000	1111111111111111	0	0	1	1	1	1	0000000000000000	1	0
0000000000000000	1111111111111111	1	1	0	0	1	1	0000000000000001	0	0
0000000000000000	1111111111111111	0	1	1	1	1	1	0000000000000001	0	0
0000000000000000	1111111111111111	1	1	0	1	1	1	0000000000000000	1	0
0000000000000000	1111111111111111	0	0	1	1	1	0	1111111111111111	0	1
0000000000000000	1111111111111111	1	1	0	0	1	0	1111111111111110	0	1
0000000000000000	1111111111111111	0	0	0	0	1	0	1111111111111111	0	1
0000000000000000	1111111111111111	0	1	0	0	1	1	0000000000000001	0	0
0000000000000000	1111111111111111	0	0	0	1	1	1	1111111111111111	0	1
0000000000000000	1111111111111111	0	0	0	0	0	0	0000000000000000	1	0
0000000000000000	1111111111111111	0	1	0	1	0	1	1111111111111111	0	1
000000000010001	0000000000000011	1	0	1	0	1	0	0000000000000000	1	0
000000000010001	0000000000000011	1	1	1	1	1	1	0000000000000001	0	0
000000000010001	0000000000000011	1	1	1	0	1	0	1111111111111111	0	1
000000000010001	0000000000000011	0	0	1	1	0	0	000000000010001	0	0
000000000010001	0000000000000011	1	1	0	0	0	0	0000000000000011	0	0
000000000010001	0000000000000011	0	0	1	1	0	1	1111111111101110	0	1
000000000010001	0000000000000011	1	1	0	0	0	1	1111111111111100	0	1
000000000010001	0000000000000011	0	0	1	1	1	1	1111111111101111	0	1
000000000010001	0000000000000011	1	1	0	0	1	1	1111111111111101	0	1
000000000010001	0000000000000011	0	1	1	1	1	1	0000000000010010	0	0
000000000010001	0000000000000011	1	1	0	1	1	1	0000000000000100	0	0
000000000010001	0000000000000011	0	0	1	1	1	0	0000000000010000	0	0
000000000010001	0000000000000011	1	1	0	0	1	0	0000000000000010	0	0
000000000010001	0000000000000011	0	0	0	0	1	0	0000000000010100	0	0
000000000010001	0000000000000011	0	1	0	0	1	1	0000000000001110	0	0
000000000010001	0000000000000011	0	0	0	1	1	1	1111111111110010	0	1
000000000010001	0000000000000011	0	0	0	0	0	0	0000000000000001	0	0
000000000010001	0000000000000011	0	1	0	1	0	1	0000000000010011	0	0

BIT

```
CHIP Bit {
    IN in, load;
    OUT out;

    PARTS:
        Mux(a=t1, b=in, sel=load, out=w1);
        DFF(in=w1, out=t1, out=out);
}
```

REGISTER

```
CHIP Register {
    IN in[16], load;
    OUT out[16];

    PARTS:
        Bit(in=in[0], load=load, out=out[0]);
        Bit(in=in[1], load=load, out=out[1]);
        Bit(in=in[2], load=load, out=out[2]);
        Bit(in=in[3], load=load, out=out[3]);
        Bit(in=in[4], load=load, out=out[4]);
        Bit(in=in[5], load=load, out=out[5]);
        Bit(in=in[6], load=load, out=out[6]);
        Bit(in=in[7], load=load, out=out[7]);
        Bit(in=in[8], load=load, out=out[8]);
        Bit(in=in[9], load=load, out=out[9]);
        Bit(in=in[10], load=load, out=out[10]);
        Bit(in=in[11], load=load, out=out[11]);
        Bit(in=in[12], load=load, out=out[12]);
        Bit(in=in[13], load=load, out=out[13]);
        Bit(in=in[14], load=load, out=out[14]);
        Bit(in=in[15], load=load, out=out[15]);
}
```

PC

```
CHIP PC {
  IN in[16], load, inc, reset;
  OUT out[16];

  PARTS:
    Or8Way(in[0]=load, in[1]=inc, in[2]=reset, in[3..7]=false, out=l1);

    Inc16(in=w1, out=w2);
    Mux16(a=w2, b=in, sel=load, out=w3);
    Mux16(a=w3, b=false, sel=reset, out=w4);

    Register(in=w4, load=l1, out=w1, out=out);
}
```

RAM8

```
CHIP RAM8 {
  IN in[16], load, address[3];
  OUT out[16];

  PARTS:
    DMux8Way16(in=in, sel=address, a=t1, b=t2, c=t3, d=t4, e=t5, f=t6, g=t7, h=t8);
    DMux8Way(in=load, sel=address, a=l1, b=l2, c=l3, d=l4, e=l5, f=l6, g=l7, h=l8);
    Register(in=t1, load=l1, out=w1);
    Register(in=t2, load=l2, out=w2);
    Register(in=t3, load=l3, out=w3);
    Register(in=t4, load=l4, out=w4);
    Register(in=t5, load=l5, out=w5);
    Register(in=t6, load=l6, out=w6);
    Register(in=t7, load=l7, out=w7);
    Register(in=t8, load=l8, out=w8);
    Mux8Way16(a=w1, b=w2, c=w3, d=w4, e=w5, f=w6, g=w7, h=w8, sel=address, out=out);
}
```

RAM64

```
CHIP RAM64 {
  IN in[16], load, address[6];
  OUT out[16];

  PARTS:
    DMux8Way(in=load, sel=address[3..5], a=l1, b=l2, c=l3, d=l4, e=l5, f=l6, g=l7, h=l8);
    RAM8(in=in, load=l1, address=address[0..2], out=t1);
    RAM8(in=in, load=l2, address=address[0..2], out=t2);
    RAM8(in=in, load=l3, address=address[0..2], out=t3);
    RAM8(in=in, load=l4, address=address[0..2], out=t4);
    RAM8(in=in, load=l5, address=address[0..2], out=t5);
    RAM8(in=in, load=l6, address=address[0..2], out=t6);
    RAM8(in=in, load=l7, address=address[0..2], out=t7);
    RAM8(in=in, load=l8, address=address[0..2], out=t8);
    Mux8Way16(a=t1, b=t2, c=t3, d=t4, e=t5, f=t6, g=t7, h=t8, sel=address[3..5], out=out);
}
```

HACK CPU

```
CHIP CPU {

    IN inM[16],          // M value input (M = contents of RAM[A])
        instruction[16], // Instruction for execution
        reset;           // Signals whether to re-start the current program
                        // (reset == 1) or continue executing the current
                        // program (reset == 0).

    OUT outM[16],         // M value output
        writeM,          // Write into M?
        addressM[15],    // RAM address (of M)
        pc[15];          // ROM address (of next instruction)

    PARTS:
        PC(in=outa, load=jump, inc=true, reset=reset, out[0..14]=pc);

        And(a=instruction[15], b=true, out=cinst);
        And(a=instruction[12], b=cinst, out=minst);
        Not(in=cinst, out=ainst);

        And(a=instruction[5], b=cinst, out=storea);
        And(a=instruction[4], b=cinst, out=stored);
        And(a=instruction[3], b=cinst, out=storem, out=writeM);

        And(a=instruction[2], b=cinst, out=instjmplt);
        And(a=instruction[1], b=cinst, out=instjmpeq);
        And(a=instruction[0], b=cinst, out=instjmpgt);

        DRegister(in=outalu, load=stored, out=outd);

        Or(a=ainst, b=storea, out=loada);
        Mux16(a=instruction, b=outalu, sel=storea, out=ina);
        ARegister(in=ina, load=loada, out=outa, out[0..14]=addressM);

        Mux16(a=outa, b=inM, sel=minst, out=outaorm);

        ALU(x=outd, y=outaorm, zx=instruction[11], nx=instruction[10],
            zy=instruction[9], ny=instruction[8], f=instruction[7],
            no=instruction[6], zr=aluzr, ng=alung, out=outM, out=outalu);

        Not(in=alung, out=notalung);
        Not(in=aluzr, out=notaluzr);
        And(a=notalung, b=notaluzr, out=alupv);
        And(a=instjmplt, b=alung, out=jumplt);
        And(a=instjmpeq, b=aluzr, out=jumpeq);
        And(a=instjmpgt, b=alupv, out=jumpgt);
        Or8Way(in[0]=jumplt, in[1]=jumpeq, in[2]=jumpgt, in[3..7]=false, out=jump);

}
```

OUTPUT

time	inM	instruction	reset	outM	writeM	addre	pc	DRegiste
0+	0	0011000000111001	0	0	0	0	0	0
1	0	0011000000111001	0	0	0	12345	1	0
1+	0	1110110000010000	0	12345	0	12345	1	12345
2	0	1110110000010000	0	12345	0	12345	2	12345
2+	0	0101101110100000	0	-1	0	12345	2	12345
3	0	0101101110100000	0	-1	0	23456	3	12345
3+	0	1110000111010000	0	11111	0	23456	3	11111
4	0	1110000111010000	0	12345	0	23456	4	11111
4+	0	0000001111101000	0	-11111	0	23456	4	11111
5	0	0000001111101000	0	-11111	0	1000	5	11111
5+	0	1110001100001000	0	11111	1	1000	5	11111
6	0	1110001100001000	0	11111	1	1000	6	11111
6+	0	0000001111101001	0	-11111	0	1000	6	11111
7	0	0000001111101001	0	-11111	0	1001	7	11111
7+	0	1110001110011000	0	11110	1	1001	7	11110
8	0	1110001110011000	0	11109	1	1001	8	11110
8+	0	0000001111101000	0	-11110	0	1001	8	11110
9	0	0000001111101000	0	-11110	0	1000	9	11110
9+	11111	1111010011010000	0	-1	0	1000	9	-1
10	11111	1111010011010000	0	-11112	0	1000	10	-1
10+	11111	0000000000001110	0	1000	0	1000	10	-1
11	11111	0000000000001110	0	14	0	14	11	-1
11+	11111	1110001100000100	0	-1	0	14	11	-1
12	11111	1110001100000100	0	-1	0	14	14	-1
12+	11111	0000001111100111	0	1	0	14	14	-1
13	11111	0000001111100111	0	1	0	999	15	-1
13+	11111	1110110111100000	0	1000	0	999	15	-1
14	11111	1110110111100000	0	1001	0	1000	16	-1
14+	11111	1110001100001000	0	-1	1	1000	16	-1
15	11111	1110001100001000	0	-1	1	1000	17	-1
15+	11111	00000000000010101	0	1000	0	1000	17	-1
16	11111	00000000000010101	0	21	0	21	18	-1
16+	11111	11100111111000010	0	0	0	21	18	-1
17	11111	11100111111000010	0	0	0	21	21	-1
17+	11111	0000000000000010	0	21	0	21	21	-1
18	11111	0000000000000010	0	2	0	2	22	-1
18+	11111	1110000010010000	0	1	0	2	22	1
19	11111	1110000010010000	0	3	0	2	23	1
19+	11111	0000001111101000	0	-1	0	2	23	1
20	11111	0000001111101000	0	-1	0	1000	24	1
20+	11111	1110111010010000	0	-1	0	1000	24	-1
21	11111	1110111010010000	0	-1	0	1000	25	-1
21+	11111	1110001100000001	0	-1	0	1000	25	-1
22	11111	1110001100000001	0	-1	0	1000	26	-1
22+	11111	1110001100000010	0	-1	0	1000	26	-1
23	11111	1110001100000010	0	-1	0	1000	27	-1
23+	11111	1110001100000011	0	-1	0	1000	27	-1
24	11111	1110001100000011	0	-1	0	1000	28	-1
24+	11111	1110001100000100	0	-1	0	1000	28	-1
25	11111	1110001100000100	0	-1	0	1000	1000	-1

25+	11111	1110001100000101	0	-1	0	1000	1000	-1
26	11111	1110001100000101	0	-1	0	1000	1000	-1
26+	11111	1110001100000110	0	-1	0	1000	1000	-1
27	11111	1110001100000110	0	-1	0	1000	1000	-1
27+	11111	1110001100000111	0	-1	0	1000	1000	-1
28	11111	1110001100000111	0	-1	0	1000	1000	-1
28+	11111	1110101010010000	0	0	0	1000	1000	0
29	11111	1110101010010000	0	0	0	1000	1001	0
29+	11111	1110001100000001	0	0	0	1000	1001	0
30	11111	1110001100000001	0	0	0	1000	1002	0
30+	11111	1110001100000010	0	0	0	1000	1002	0
31	11111	1110001100000010	0	0	0	1000	1000	0
31+	11111	1110001100000011	0	0	0	1000	1000	0
32	11111	1110001100000011	0	0	0	1000	1000	0
32+	11111	1110001100000100	0	0	0	1000	1000	0
33	11111	1110001100000100	0	0	0	1000	1001	0
33+	11111	1110001100000101	0	0	0	1000	1001	0
34	11111	1110001100000101	0	0	0	1000	1002	0
34+	11111	1110001100000110	0	0	0	1000	1002	0
35	11111	1110001100000110	0	0	0	1000	1000	0
35+	11111	1110001100000111	0	0	0	1000	1000	0
36	11111	1110001100000111	0	0	0	1000	1000	0
36+	11111	1110111111010000	0	1	0	1000	1000	1
37	11111	1110111111010000	0	1	0	1000	1001	1
37+	11111	1110001100000001	0	1	0	1000	1001	1
38	11111	1110001100000001	0	1	0	1000	1000	1
38+	11111	1110001100000010	0	1	0	1000	1000	1
39	11111	1110001100000010	0	1	0	1000	1001	1
39+	11111	1110001100000011	0	1	0	1000	1001	1
40	11111	1110001100000011	0	1	0	1000	1000	1
40+	11111	1110001100000100	0	1	0	1000	1000	1
41	11111	1110001100000100	0	1	0	1000	1001	1
41+	11111	1110001100000101	0	1	0	1000	1001	1
42	11111	1110001100000101	0	1	0	1000	1000	1
42+	11111	1110001100000110	0	1	0	1000	1000	1
43	11111	1110001100000110	0	1	0	1000	1001	1
43+	11111	1110001100000111	0	1	0	1000	1001	1
44	11111	1110001100000111	0	1	0	1000	1000	1
44+	11111	1110001100000111	1	1	0	1000	1000	1
45	11111	1110001100000111	1	1	0	1000	0	1
45+	11111	0111111111111111	0	1	0	1000	0	1
46	11111	0111111111111111	0	1	0	32767	1	1

DESIGN AND IMPLEMENT A SYNCHRONOUS COUNTER THAT COUNTS DOWN FROM DECIMAL DIGIT 9 TO 0

Introduction:

A 4-bit 9-0 Synchronous Counter is a digital circuit that counts in a binary sequence from 9 to 0 and then resets to 9, essentially counting decimal digits from 9 to 0. It's built using flip-flops, which change states in synchronization with the clock signal, ensuring all bits update at the same time. Synchronous counters have several advantages over asynchronous counters, including reduced propagation delays and increased reliability at higher clock frequencies. These counters find applications in digital clocks, timers, and other devices requiring precise counting.

This project aims to design and implement a 4-bit synchronous counter that limits the counting to a range from 9 to 0 (binary sequence 1001 to 0000). Such a counter is also known as a decade counter because it counts ten states. Beyond the zeroth count (0000), the counter resets to zero on the next clock pulse.

Objectives:


Understand the fundamentals of synchronous counters - Gain insight into how synchronous counters differ from asynchronous counters, focusing on the use of a clock pulse to synchronize state changes.

Design a 4-bit binary counter circuit - Develop a binary counter using JK flip-flops to count sequentially from 9 to 0.

Implement a reset mechanism - Ensure the counter resets back to 0 after reaching the binary equivalent of 9 (1001).

Analyse applications - Explore the practical applications of synchronous counters in devices requiring controlled counting mechanisms, such as digital clocks, frequency dividers, and electronic timers.

 BLOCK DIAGRAM FOR MOD-10 SYNCHRONOUS DOWN COUNTER




TRUTH TABLE

Present State				Next State				J _A	K _A	J _B	K _B	J _C	K _C	J _D	K _D
Q _A	Q _B	Q _C	Q _D	Q _{A+1}	Q _{B+1}	Q _{C+1}	Q _{D+1}								
1	0	0	1	1	0	0	1	x	0	0	x	0	x	x	1
1	0	0	0	0	1	1	1	x	1	1	x	1	x	1	x
0	1	1	1	0	1	1	0	0	x	x	0	x	0	x	1
0	1	1	0	0	1	0	1	0	x	x	0	x	1	1	x
0	1	0	1	0	1	0	0	0	x	x	0	0	x	x	1
0	1	0	0	0	0	1	1	0	x	x	1	1	x	1	x
0	0	1	1	0	0	1	0	0	x	0	x	x	0	x	1
0	0	1	0	0	0	0	1	0	x	0	x	x	1	1	x
0	0	0	1	0	0	0	0	0	x	0	x	0	x	x	1
0	0	0	0	1	0	0	1	1	x	0	x	0	x	1	x

X → Don't care

STATE DIAGRAM

 

K-MAPS

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	1			
01				
11				
10	X	X		

$$J_A = \bar{Q}_B \bar{Q}_C \bar{Q}_D$$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00				
01	X	X	X	X
11				
10	1			

$$J_B = Q_A \bar{Q}_B \bar{Q}_C \bar{Q}_D$$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00			X	X
01	1		X	X
11				
10	1			

$$J_C = \bar{Q}_A \bar{Q}_B \bar{Q}_D + Q_A \bar{Q}_B \bar{Q}_C \bar{Q}_D$$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11				
10	1			

$$K_A = \bar{Q}_B \bar{Q}_C \bar{Q}_D$$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X		X
01	1			
11				
10	X	X		

$$K_B = \bar{Q}_A \bar{Q}_C \bar{Q}_D$$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X		1
01	X	X		1
11				
10	X	X		

$$K_C = \bar{Q}_A \bar{Q}_D$$

GATES USED

AND3

```
CHIP And3{  
    IN a,b,c;  
    OUT out;  
  
    PARTS:  
    And(a=a,b=b,out=a1);  
    And(a=a1,b=c,out=out);  
}
```

JK FLIP FLOP USING D FLIP FLOP

```
CHIP JKusingD{  
    IN J,K;  
    OUT Q;  
    PARTS:  
    Not(in=K,out=kbar);  
    And(a=kbar,b=q,out=x1);  
    Not(in=q,out=notq);  
    And(a=J,b=notq,out=x2);  
    Or(a=x1,b=x2,out=y);  
    DFF(in=y,out=q,out=Q);  
  
}
```

MOD10

```
CHIP MOD10{
  OUT out[4];
  PARTS:
    Not(in=q1,out=q1bar);
    Not(in=q2,out=q2bar);
    Not(in=q3,out=q3bar);
    Not(in=q4,out=q4bar);

    And3(a=q2bar,b=q3bar,c=q4bar,out=J1);
    And3(a=q1,b=q2bar,c=q3bar,out=x);
    And(a=q4bar,b=x,out=J2);
    And3(a=q1bar,b=q2,c=q4bar,out=y);
    And(a=q1,b=J1,out=z);
    Or(a=y,b=z,out=J3);

    And3(a=q2bar,b=q3bar,c=q4bar,out=K1);
    And3(a=q1bar,b=q3bar,c=q4bar,out=K2);
    And(a=q1bar,b=q4bar,out=K3);

    JKusingD(J=true,K=true,Q=q4,Q=out[0]);
    JKusingD(J=J3,K=K3,Q=q3,Q=out[1]);
    JKusingD(J=J2,K=K2,Q=q2,Q=out[2]);
    JKusingD(J=J1,K=K1,Q=q1,Q=out[3]);
}
```

OUTPUT

Hardware Simulator (2.5) - D:\DJT\Downloads\PROJECTS\MINE\EOC\1\MOD10.hdl

File View Run Help

Slow Fast

Chip Name : Time : 30

Input pins		Output pins	
Name	Value	Name	Value
		out [4]	6

HDL		Internal pins	
		Name	Value
CHIP MOD10{		q1	0
OUT out [4];		q1bar	1
PARTS:		q2	1
Not (in=q1, out=q1bar);		q2bar	0
Not (in=q2, out=q2bar);		q3	1
Not (in=q3, out=q3bar);		q3bar	0
Not (in=q4, out=q4bar);		q4	0
And3 (a=q2bar, b=q3bar, c=q4bar, out=x);		q4bar	1
And3 (a=q1, b=q2bar, c=q3bar, out=y);		J1	0
And (a=q4bar, b=x, out=J2);		x	0
And3 (a=q1bar, b=q2, c=q4bar, out=z);		J2	0
And (a=q1, b=J1, out=z);		y	1
Or (a=y, b=z, out=J3);		z	0
		J3	1

CONCLUSION

We have designed and implemented a HACK CPU. The Hack CPU is the target for the Jack language compiler later in the course. By compiling Jack code to Hack machine language, students see how high-level code translates to machine-level operations, solidifying their understanding of compilation and CPU operation.

We have also designed and implemented a SYNCHRONOUS COUNTER that counts down from DECIMAL DIGIT 9 TO 0. This type of counter is useful for visual countdowns, such as those seen on display boards at events, sports arenas, or conferences, where it counts down each second or minute. It is often coupled with a display to show the countdown, providing a visual cue that counts down from a set time until an event, like the start of a race or a break in a program. Many household and consumer devices use down counters in settings like microwave timers, washing machine cycles, or cooking timers, decrementing through a sequence until the task completes. Since all flip-flops in a synchronous counter are triggered simultaneously, they offer a predictable and stable output, ideal for precise applications. Synchronous counters are faster than asynchronous counters because they do not suffer from propagation delay between stages, making them suitable for high-speed digital applications.